

# EEE 108L MICRO-ELECTRONICS 1

## LAB 3

**Lab Session: Tuesday 3PM - 5:40PM**

**Student Name: Andrew Robertson**

## TABLE OF CONTENTS

PRE-LAB Calculations .....	3
Step 1.....	3
Step 2.....	3
Step 3.....	3
Step 4.....	3
SPICE Simulation.....	4
Step 5.....	4
Step 6.....	5
Step 7.....	6
Step 8.....	6
Experiment – Non-Inverting OpAmp.....	7
Step 9.....	7
Step 10.....	7
Step 11.....	8
Step 12.....	9
Experiment – Inverting OpAmp.....	10
Step 13.....	10
Step 14.....	10
Step 15.....	11
Step 16.....	12
Step 17.....	12
Conclusions.....	13
Appendix A .....	15

## PRE-LAB CALCULATIONS

STEP 1.

$$Av1 = \frac{Rb}{Ra} + 1$$

Ra has been selected as 10kΩ, leaving Rb to be 20kΩ to meet spec.

This selection allows Av1 to be exactly 3V/V

(Please see figure 1 in appendix A for complete calculations)

STEP 2.

$$VN1 = Vout \left( \frac{Ra}{Ra + Rb} \right)$$

Rin is infinite.

(Please see figure 1 in appendix A for complete calculations)

STEP 3.

$$Av2 = -\frac{Rb}{Ra}$$

Using the resistance values from before, Av2 is exactly -2V/V

(Please see figure 2 in appendix A for complete calculations)


STEP 4.

$$Rin = \frac{Rb}{2} = Ra$$

(Please see figure 2 in appendix A for complete calculations)

## SPICE SIMULATION

STEP 5.

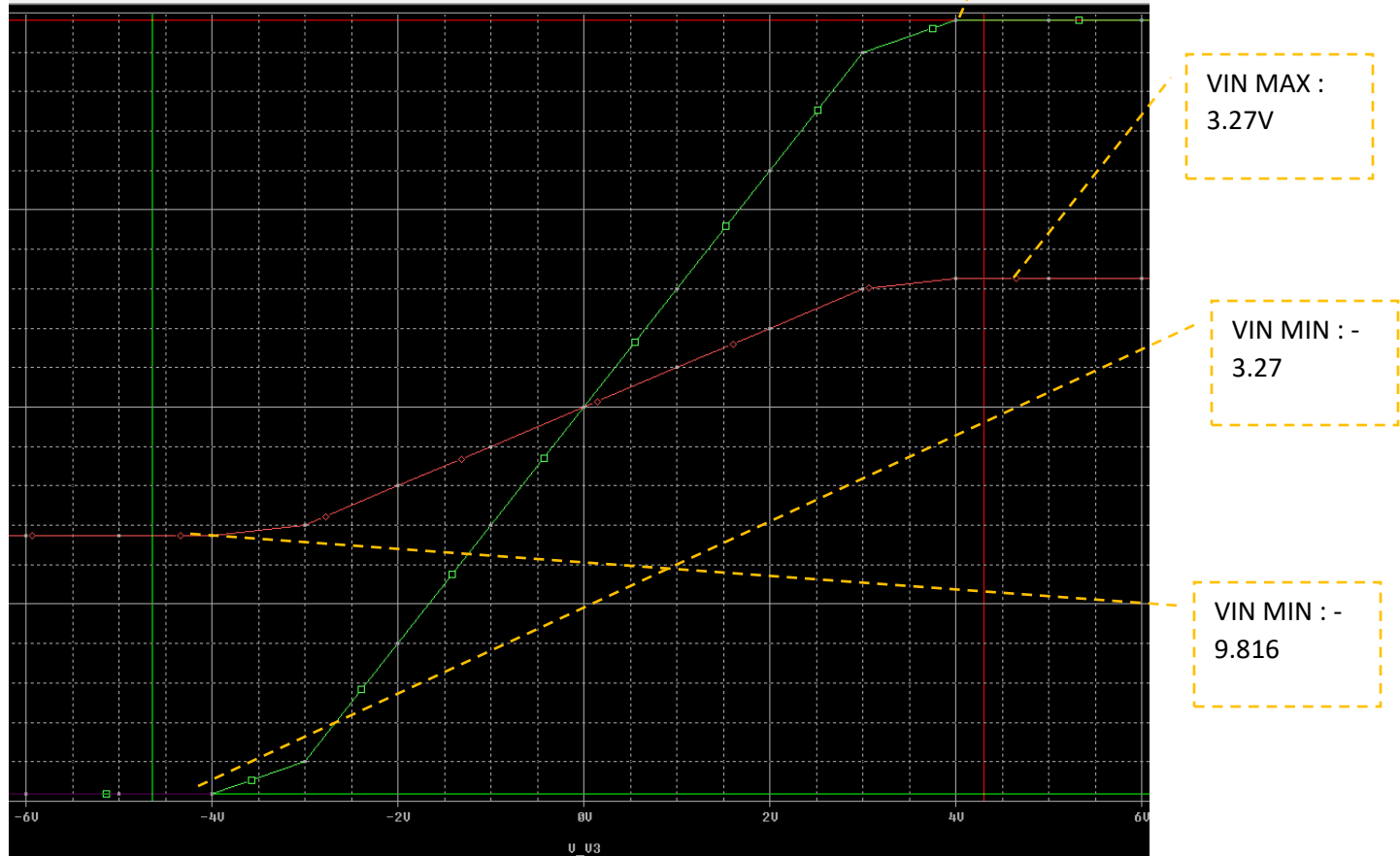

The green curve represents Vout, and the red curve is Vin. There is response from about -4V to +4V but only a stable linear response from -3V to +3V.

Placing cursors far left and right yield Vout MAX = 9.816V and Vout MIN = -9.816V

Slope during linear response

$$\frac{\Delta V_{out1}}{\Delta V_{in1}} = \frac{6.0014 + 5.9981}{1.9999 + 1.9999} = \frac{12.000}{3.9998} \cong 3V/V$$

This agrees with my prior calculations.

STEP 6.



The green curve represents  $V_{out}$ , and the red curve is  $V_{in}$ . There is stable linear response from -5V to +5V.


Placing cursors far left and right yield  $V_{out\ MAX} = 9.816V$  and  $V_{out\ MIN} = -9.816V$

Slope during linear response

$$\frac{\Delta V_{out2}}{\Delta V_{in2}} = \frac{4.9903 - 8.0015}{-2.4944 + 4.0000} = \frac{-3.0112}{1.5056} \cong -2V/V$$

This agrees with my prior calculations.

## STEP 7.

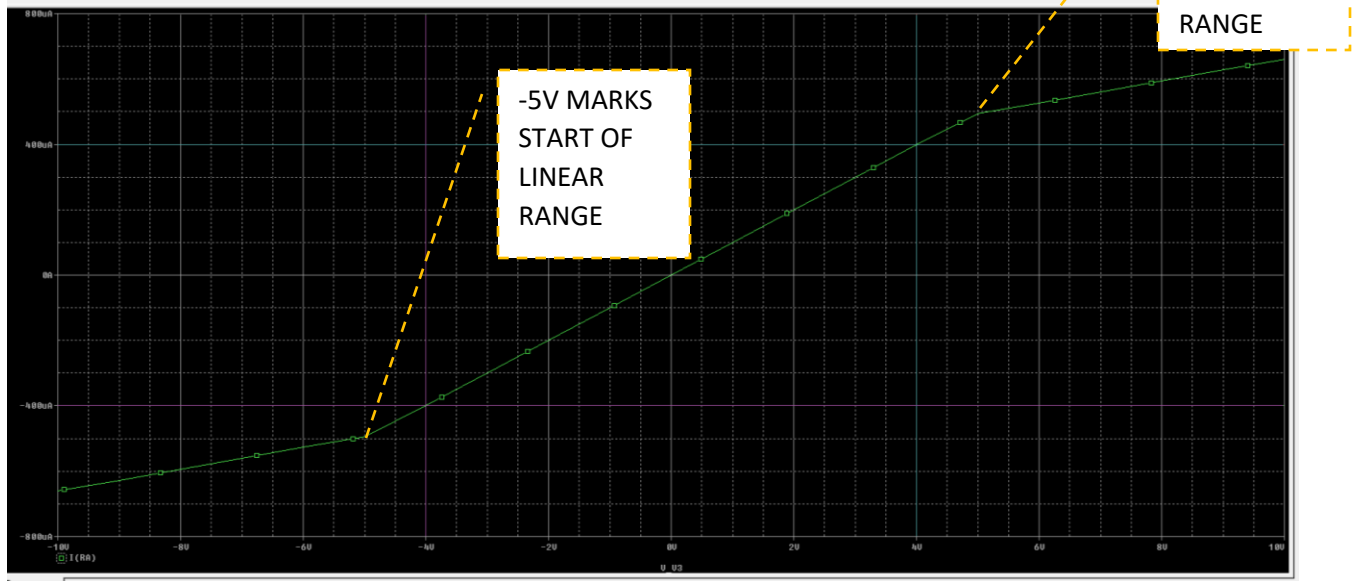

This is the current  $i_{s2}$  as a function of the  $V_{s2}$  DC sweep

$$\frac{\Delta V_{s2}}{\Delta i_{s2}} = \frac{4V + 4V}{399.994\mu + 399.998\mu} \cong 10k\Omega$$

This also agrees with my prior calculations.

## STEP 8.

The values of  $V_{out\ MAX}$  and  $V_{in\ MAX}$  regarding steps 5 and 6 are indeed the same.

We also noted  $V_n$  does not always equal  $V_p$ , this can occur when the output becomes saturated.

## EXPERIMENT – NON-INVERTING OPAMP


### STEP 9.

(No image to be shown here)

After grounding  $V_{s1}$ , our  $V_{out}$  measured 3.45 mV. The non-inverting Op-amp configuration yields a gain as follows:  $A_v = 1 + \frac{R_2}{R_1}$ . Given  $R_2 = 20.02 \text{ kohms}$  and  $R_1 = 9.91 \text{ kohms}$ , our gain is approximately 3.02 volts per volt. This means  $V_{os}$  is roughly 1.142 mV.
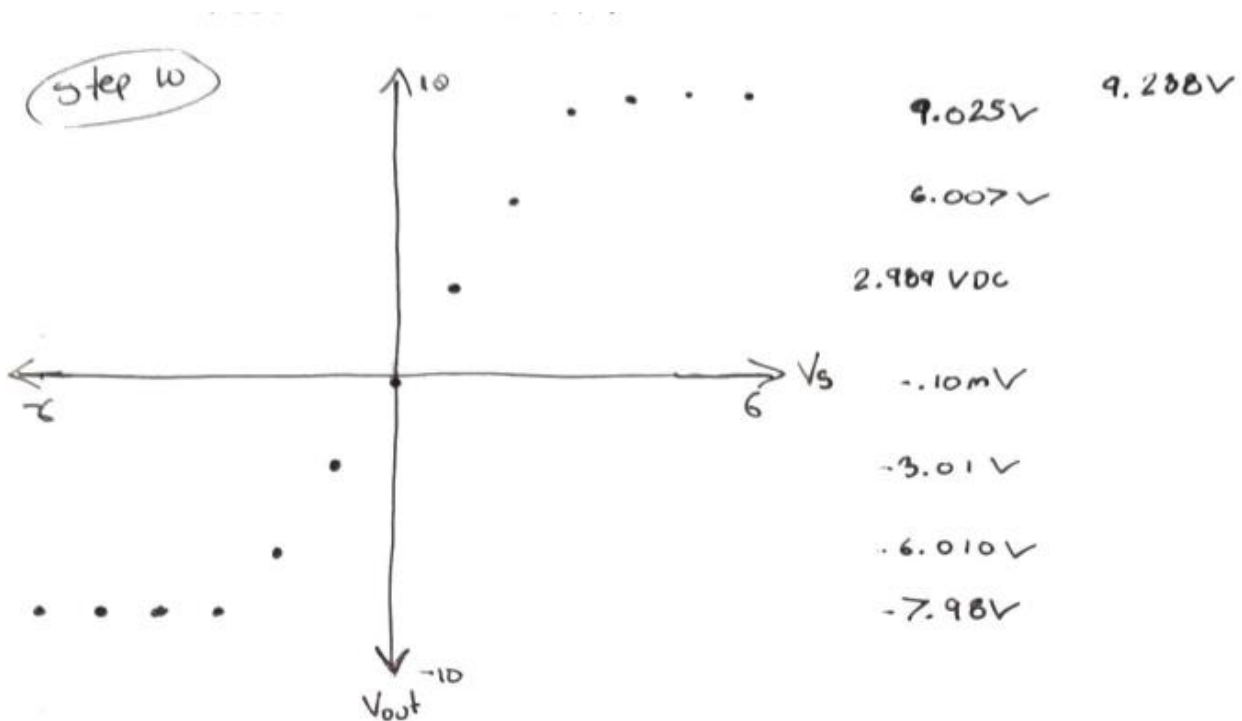
### STEP 10.

As can be seen in figure 3 of Appendix A.



Data points were taken at 1V increments starting at -6V and ending at +6V. Using data from -2V to +2V:

$$\frac{\Delta V_{out}}{\Delta V_{s1}} = \frac{6.007V + 6.010V}{2V + 2V} = \frac{12.017}{4} = 3.00425 \frac{V}{V}$$

This figure is extremely close to the calculated values of step 1, and the observed values of step 5 (both 3V/V)


$V_{out} \text{ MAX} : 9.288V$

$V_{out} \text{ MIN} : -7.98V$


STEP 11.

Vn1 MAX =  
VOUT MAX  
= 519mV

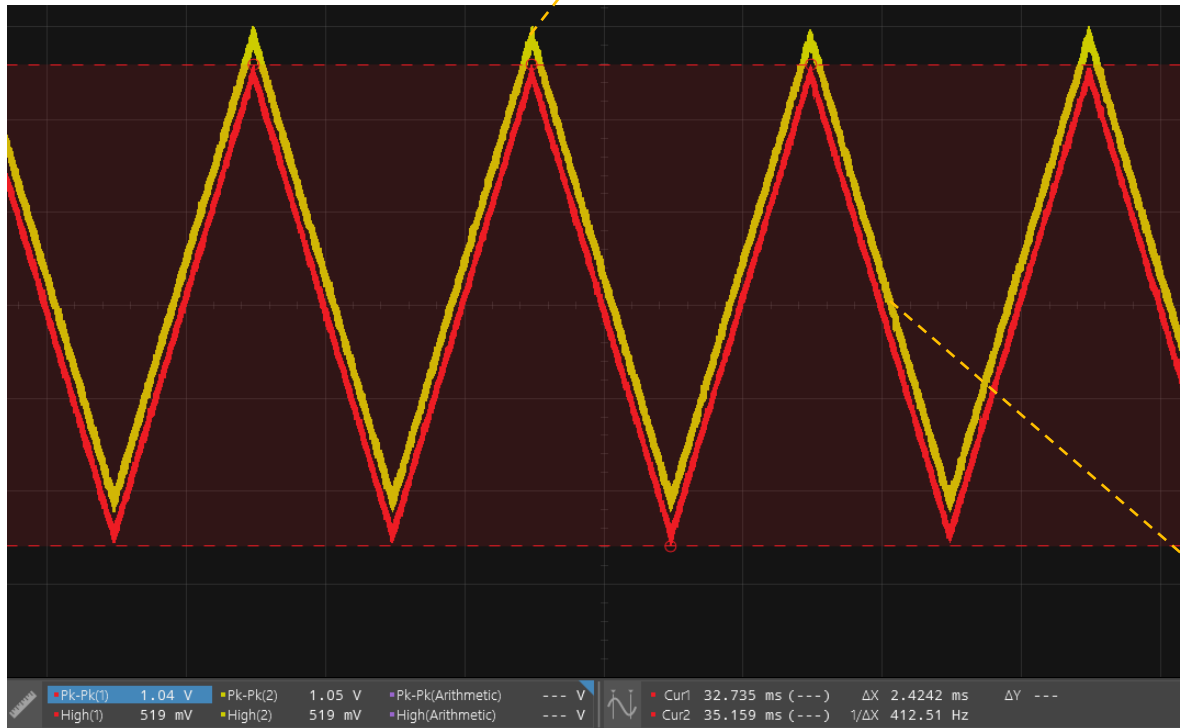The first image is Vn1 to Vout, and the second image is Vin to Vout



PEAK TO  
PEAK FOR  
BOTH IS  
1.05V

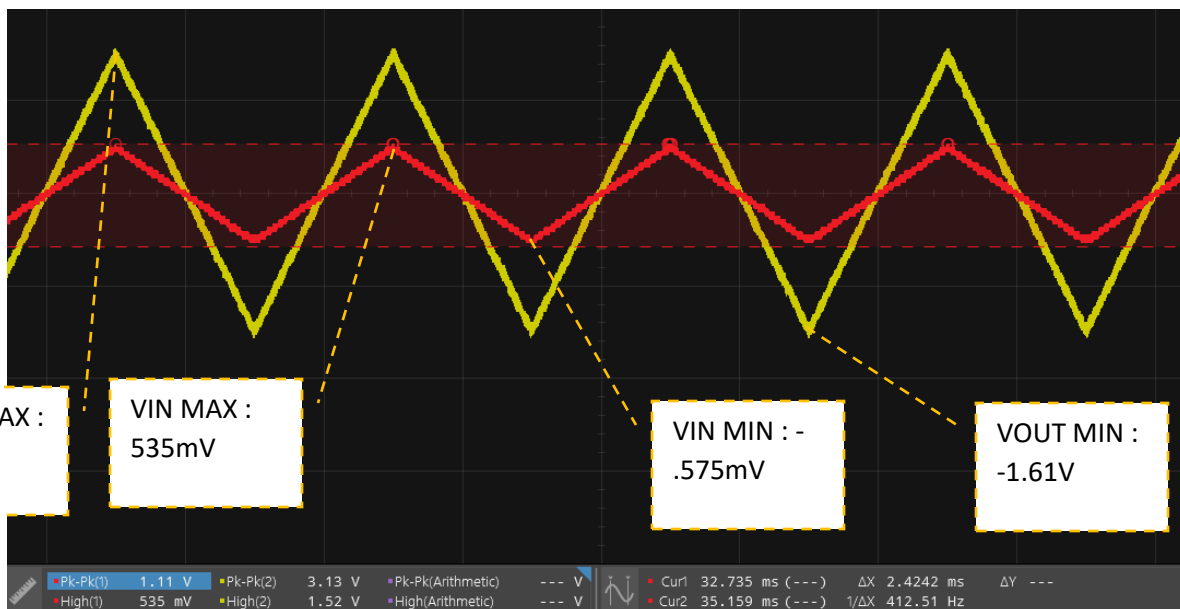

VOUT MAX :  
1.52V

VIN MAX :  
535mV

VIN MIN : -  
.575mV


VOUT MIN :  
-1.61V

Using a positive peak:

$$\frac{\Delta V_{out}}{\Delta V_{s1}} = \frac{1.52V}{535mV} = \frac{1520mV}{535mV} = 2.84112 \frac{V}{V}$$



STEP 12.

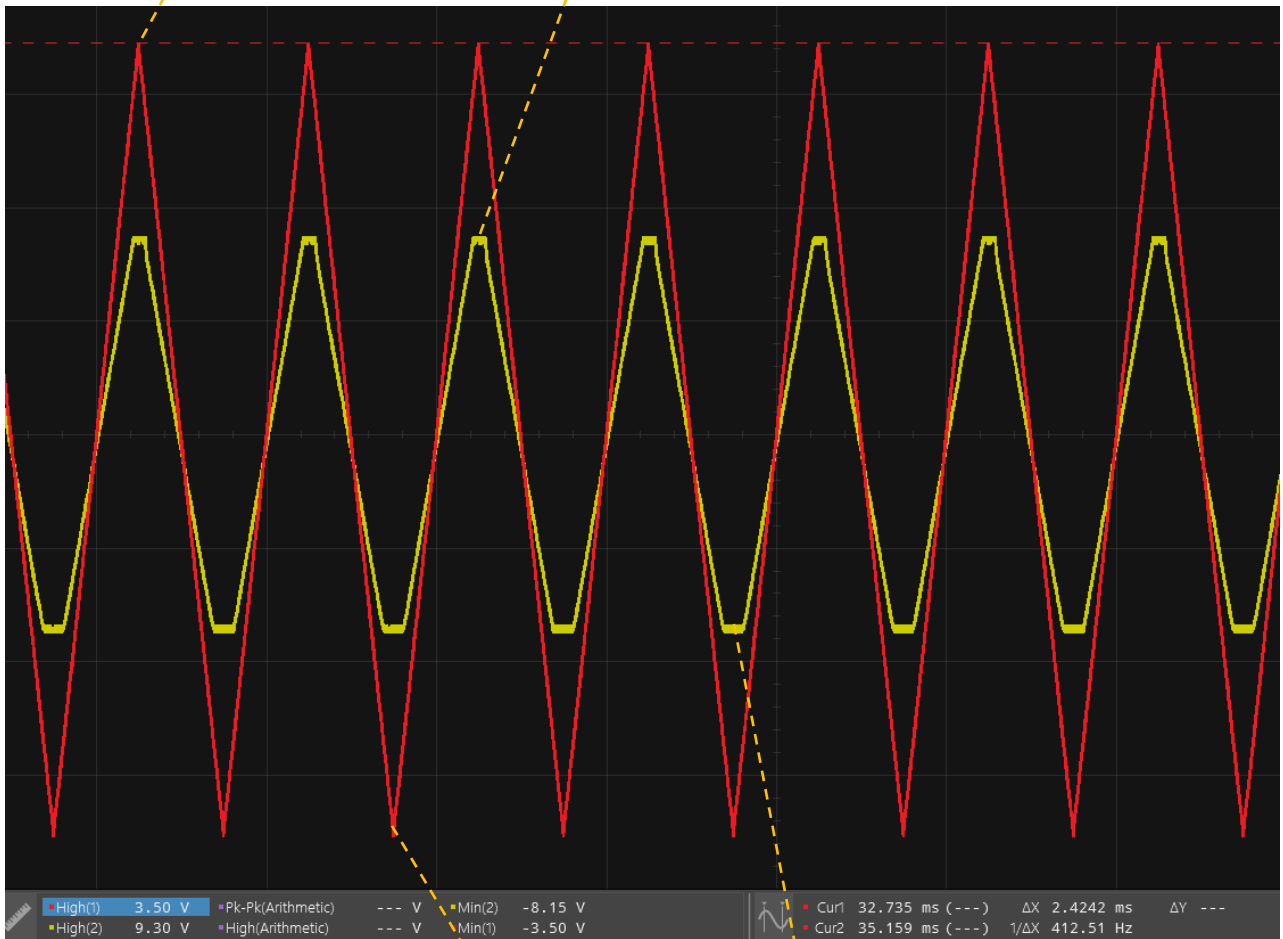VIN MAX :  
3.5VVOUT MAX :  
9.3V


Pos clipping level: 9.3V

Neg clipping level: -8.15V

VIN MIN : -  
3.5VVOUT MIN :  
-8.15V

## EXPERIMENT – INVERTING OPAMP

STEP 13.

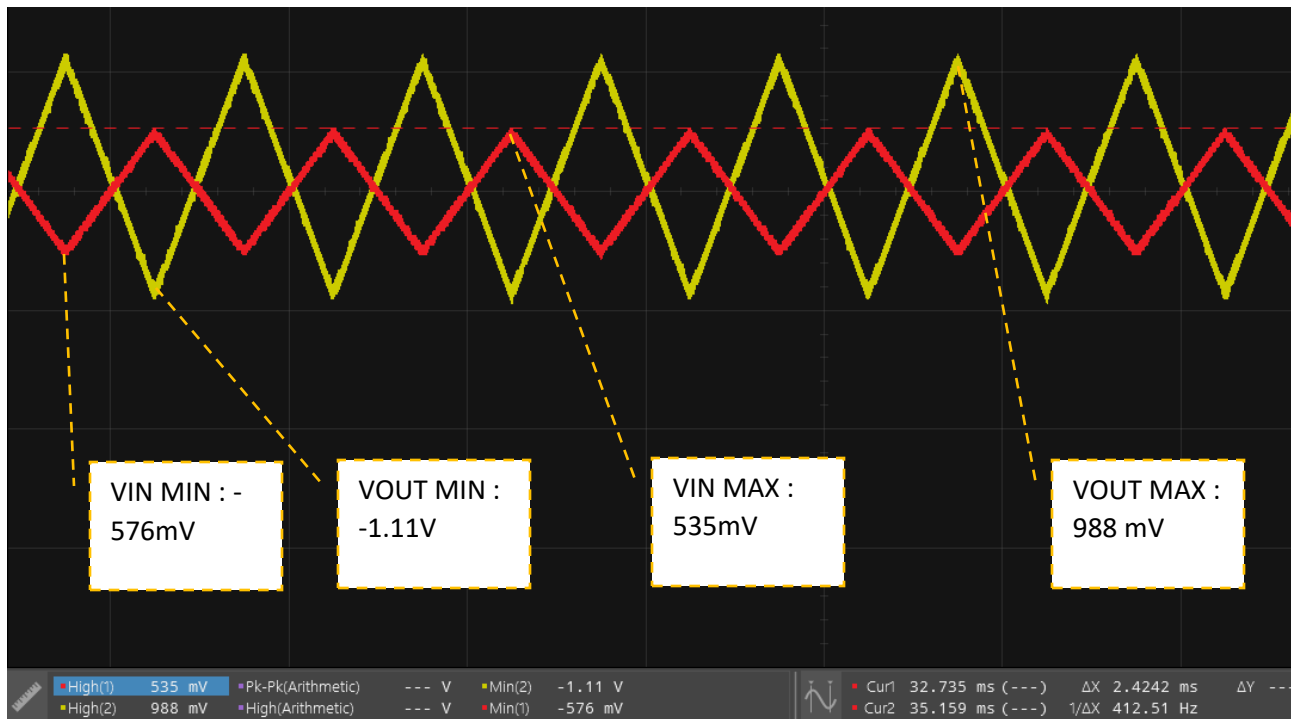


As there is no clipping here, I will use corresponding peaks for the small signal gain

$$\frac{\Delta V_{out2}}{\Delta V_{s2}} = \frac{988mV}{-535mV} = -1.8467 \frac{V}{V}$$

STEP 14.

To measure the small signal input resistance  $R_{in2}$  we first disconnected all outside sources of energy besides our reference of ground. We then used our DMM and measured from ground to the input terminal of the integrated op amp to get a value of 9.9kohms. This value is nearly the 10kohms calculated in step 4.

STEP 15.

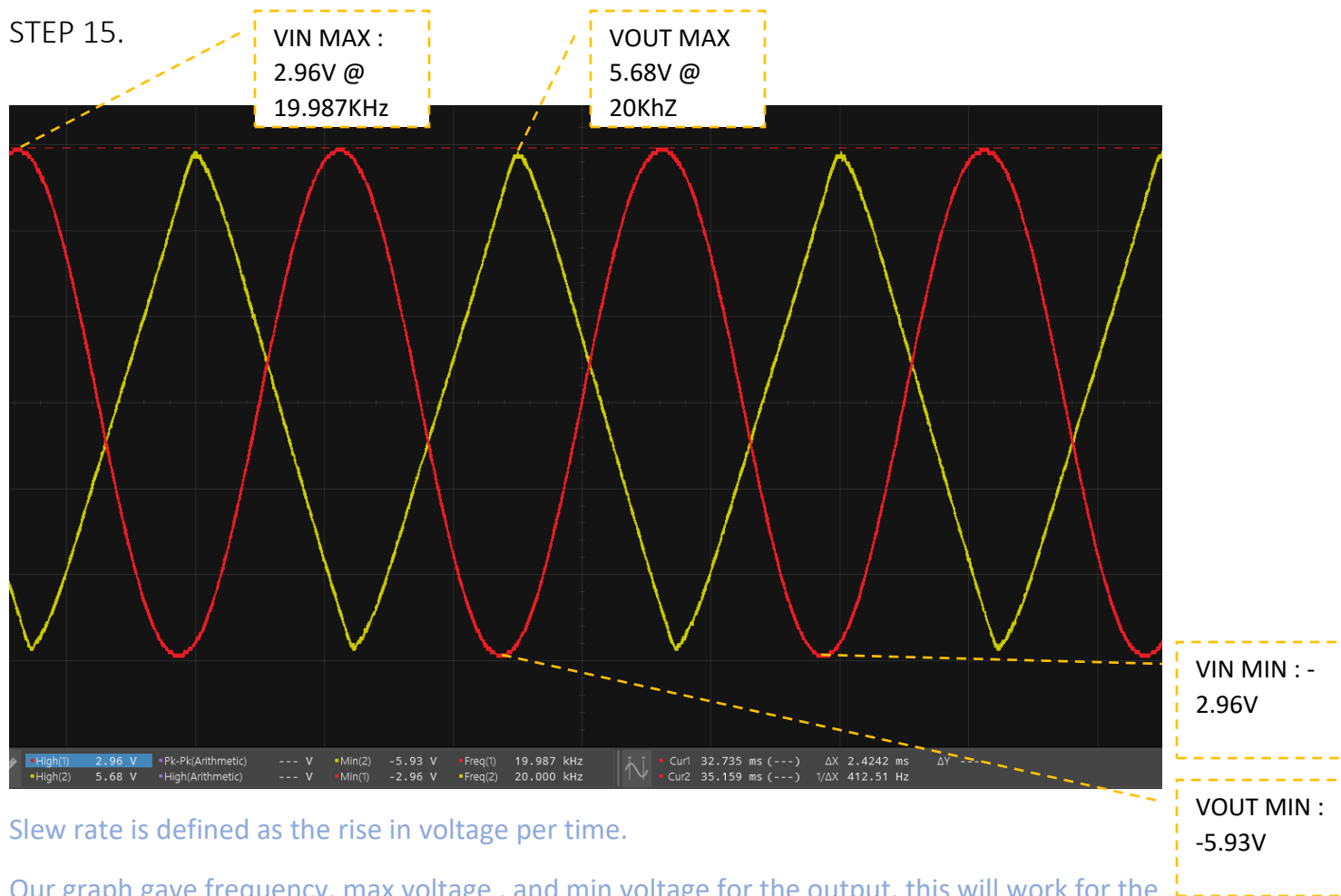


Slew rate is defined as the rise in voltage per time.

Our graph gave frequency, max voltage, and min voltage for the output, this will work for the slew rate.

$F = 1/\text{period} \Rightarrow \text{period} = 1/F = 1/20\text{kHz} = 50\text{microseconds}$ . Half of this is a single rise. One rise takes place from -5.93V to 5.68V. Total rise of 11.61V.

$$\text{slew rate} = \frac{V}{t} = \frac{11.61V}{25us} = .4644 \frac{V}{us}$$

## STEP 16.

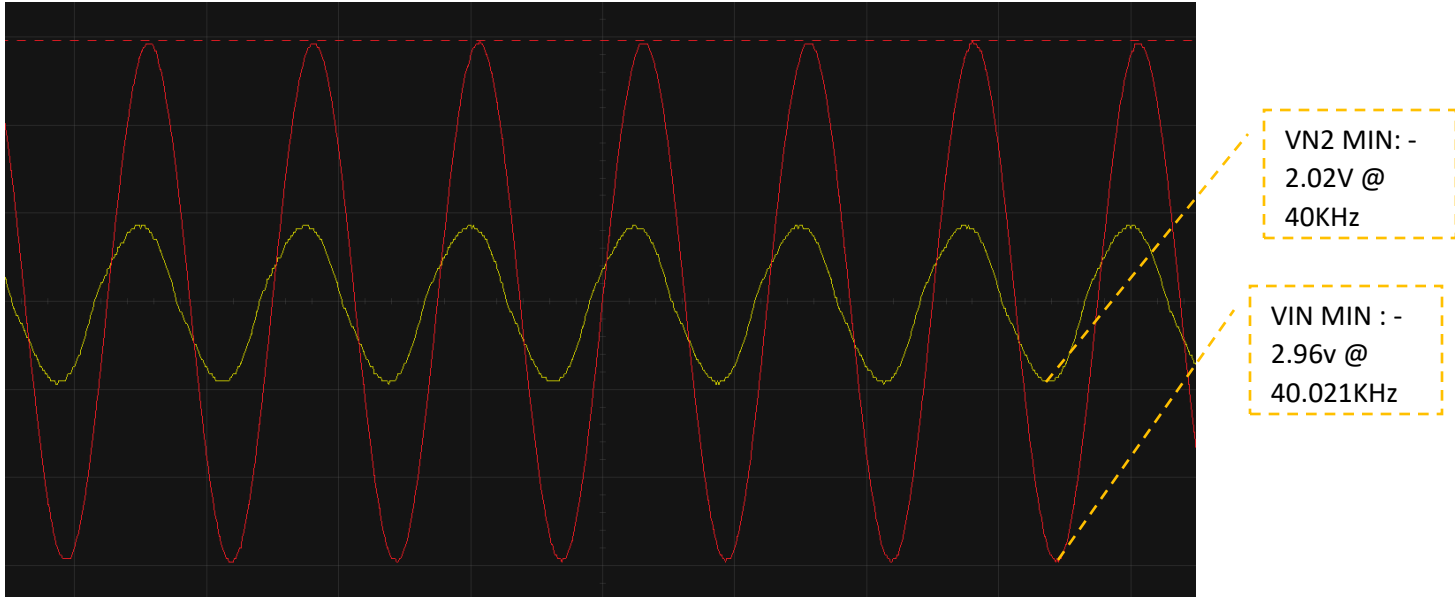

As the frequency increased, VN2 became less of a virtual ground and more of a non-negating sine wave.

## STEP 17.

(Instructed that we could not perform this part without differential mode probes)

Although As I read it again now, it seems it would have been simple to complete and the statement must have been about performing a differential measurement directly without the approach of grounding one input.

## CONCLUSIONS

### Item 1.

Compare the SPICE simulation results to the laboratory measurements with regard to gain and output clipping levels. Suggest reasons for any differences.

The SPICE simulations appear to use models much closer to ideal representations. The gain found by hand and in SPICE for the non-inverting model both came out at 3V/V exactly, yet the real-world op amp was slightly under this value, at 2.84V/V. I suspect this is because we cannot achieve ideal models in the real world, there is some sort of loss somewhere, always. The clipping levels are very near each other for the top end but off by a good amount for the bottom end. I think the bottom end issue is due to the reliance of the negative feedback for accurate results. If an output is more negative than the input, then the feedback loop doesn't really feedback.

### Item 2.

Summarize the data and calculations you did to determine the input offset voltage (VOS) of your operational amplifier. Suppose that the amplifier circuit of Figure 1 is constructed with your operational amplifier with  $R_A = 100\ \Omega$  and  $R_B = 100\ \text{k}\Omega$ . Assuming that VOS has not changed, what is the DC output voltage of the operational amplifier when the input is zero?

After grounding  $V_{s1}$ , our  $V_{out}$  measured 3.45 mV. The non-inverting Op-amp configuration yields a gain as follows:  $A_v = 1 + \frac{R_2}{R_1}$ . Given  $R_2 = 20.02\ \text{kohms}$  and  $R_1 = 9.91\ \text{kohms}$ , our gain is approximately 3.02 volts per volt. This means  $V_{os}$  is roughly 1.142 mV.

If  $R_a = R_b$  we would have a gain of 2V/V instead, given our  $V_{os}$  was calculated to be 1.142mV, the output should be 2.284mV when the input is zero.

### Item 3.

Review your data of Steps 11 and 12 and make a general statement relating the output voltage swing of an operational amplifier to its power supply voltages.

An op-amp's output cannot exceed the value of its corresponding maximum or minimum power supply voltages. The power supply voltages serve as the ceiling and floor of the outputs range.

### Item 4.

Summarize the measurements of Step 16. Multiply each measured open-loop gain by the frequency at which it was measured. The result is called the gain-bandwidth product (GBP) of the operational amplifier. Does the GBP appear to be constant for the two cases?

(We didn't complete the last part of step 16, it seems we missed reading this part)

**Item 5.**

Compare the voltage gain  $A_{dm}$  found in Step 17 with theory. Does the voltage gain  $A_{cm}$  found in Step 17 seem reasonable?

(My misinterpretation has now cost me twice)

## APPENDIX A

Figure 1.

Lab 3 Pre Lab

- Step 1.  $V_{P1} = V_{N1}$   $i_b = \frac{V_{N1} - V_{out}}{R_b}$   
 $i_a = \frac{-V_{N1}}{R_A}$

@ Node  $V_{N1}$  :  $i_a = i_b$

$$\frac{-V_{N1}}{R_A} = \frac{V_{N1} - V_{out}}{R_b} = \frac{V_{N1}}{R_b} - \frac{V_{out}}{R_b}$$

$$\frac{(R_b)(-V_{N1})}{R_A} = V_{N1} - V_{out} \quad V_{N1} = V_{s1}$$

$$\frac{(R_b)(-V_{N1})}{R_A} - V_{N1} = -V_{out}$$

$$\boxed{\frac{R_b}{R_A} + 1 = \frac{V_{out}}{V_{N1}} = A_{V_i}}$$

if we want  $A_{V_i} = 3 \frac{V}{V}$  and use  $10k\Omega$  for  $R_A$   
 then

$$\frac{R_b}{10k\Omega} + 1 = 3 \Rightarrow \frac{R_b}{10k} = 2$$

$$R_b = 20k$$

- Step 2. infinite input impedance (or zero input current)

$$R_{in} = \frac{V_{s1}}{R_{s1}}, \quad \infty = \frac{V_{s1}}{R_{s1} \rightarrow 0}$$

$V_{out} > V_{N1}$  so current flows left. Drop across  $R_A$  is  $V_{N1}$

$$\boxed{V_{N1} = V_{out} \left( \frac{R_A}{R_A + R_b} \right)}$$

Figure 2.

- Part 3

$$i_a = i_b = i_{s2} \quad i_a = \frac{V_{s2} - V_{N2}}{R_A}$$

$$V_{N2} = V_{P2}$$

$$i_b = \frac{V_{N2} - V_{out2}}{R_B}$$

$$\frac{V_{s2}}{R_A} - \frac{V_{N2}}{R_A} = \frac{V_{s2} - V_{N2}}{R_A} = \frac{V_{N2} - V_{out2}}{R_B} = \frac{V_{N2}}{R_B} - \frac{V_{out2}}{R_B}$$

$$\frac{V_{s2}}{R_A} - \frac{V_{N2}}{R_A} - \frac{V_{N2}}{R_B} = -\frac{V_{out2}}{R_B} \quad \left( \begin{array}{l} V_{P2} = 0 \text{ so} \\ V_{N2} = 0 \end{array} \right)$$

note:

$$\frac{V_{s2}}{R_A} = -\frac{V_{out2}}{R_B} \Rightarrow \boxed{\frac{-R_B}{R_A} = \frac{V_{out2}}{V_{s2}} = A_{v2}}$$

using previous values of  $R_A$  &  $R_B$ 

$$\text{we set : } \frac{-20k\Omega}{10k\Omega} = A_{v2} = -2 \checkmark$$

- Part 4

$$\text{using the gain calculated } \frac{V_{out2}}{V_{s2}} = -2 \checkmark, \quad -\frac{V_{out2}}{2} = V_{s2}$$

$$\boxed{R_{in2} = \frac{V_{s2}}{i_{s2}} = \frac{-V_{out2}}{2 i_{s2}} = \frac{-V_{out2}}{2 \left( \frac{-V_{out2}}{R_B} \right)} = \frac{R_B}{2}}$$



Figure 3.

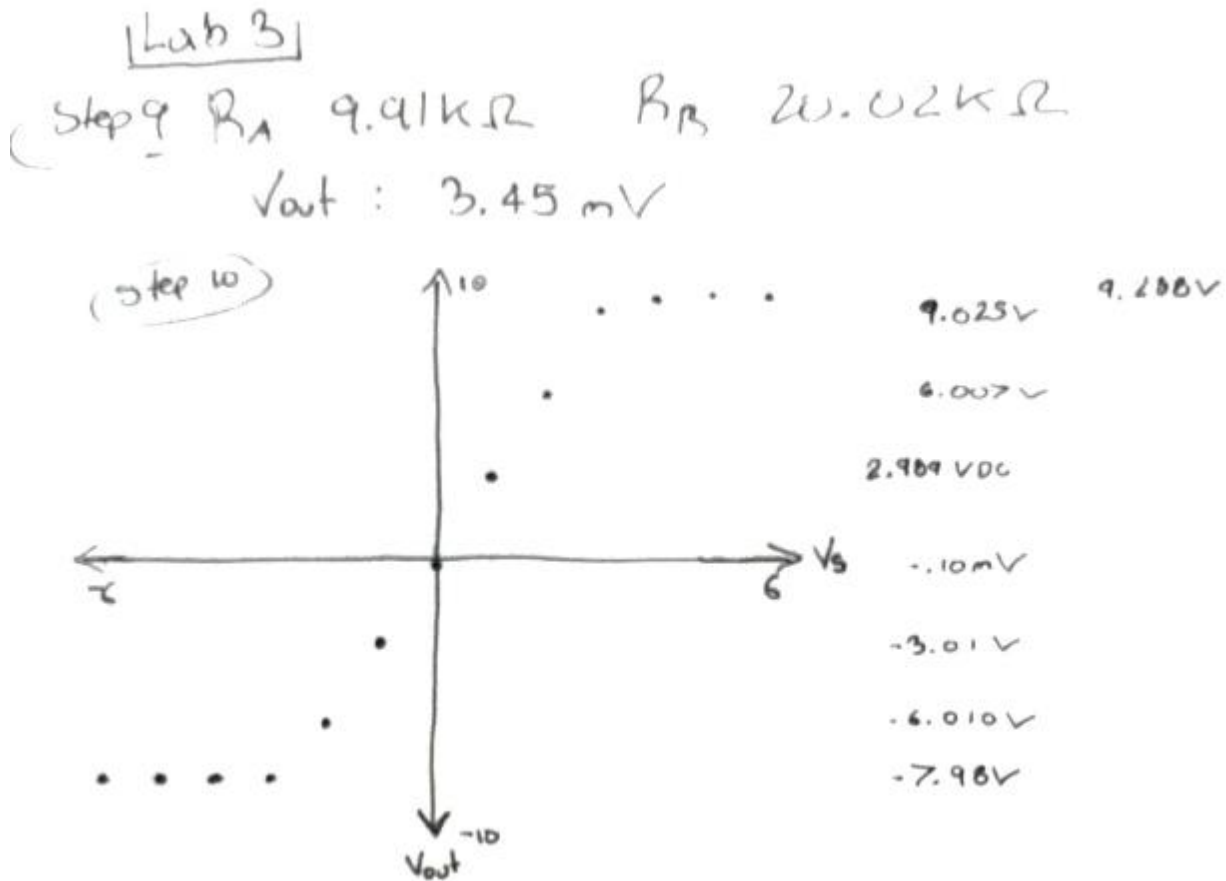


Figure 4.

Step 14  $9.9\text{ k}\Omega$  Rin 2 using  
~~pin~~ DMM (virtual bench)

Step 16 . As frequency increased  $V_{N2}$  was less of a  
 virtual ground and turned into a wave that  
 not neg+ly

Step 17

$R3 - 4.62\text{ k}$   
 $R4 - 4.63\text{ k}$   
 $R5 - 4.63\text{ k}$   
 $R6 - 4.63\text{ k}$

Step 18a

cannot do  
 no differential probe

$V_{out}$   
 $V_{in}$