

# EEE 108L MICRO-ELECTRONICS 1

## LAB 8

**Lab Session: Tuesday 3PM - 5:40PM**

**Student Name: Andrew Robertson**

## TABLE OF CONTENTS

PRE-LAB Calculations .....	3
Step 1.....	3
SPICE Simulation .....	4
Step 2.....	4
Step 3.....	5
Step 4.....	5
Step 5.....	6
Step 6.....	7
Step 7.....	7
Experiment .....	9
Step 8.....	9
Step 9.....	9
Step 10.....	10
Step 11.....	10
Conclusions.....	11
Appendix A .....	12

# PRE-LAB CALCULATIONS

## STEP 1.

(Using the steps outlined in Appendix A, Figure 1)

### Lab 8 Pre-lab

$$1) I_L = \frac{V_{pp}}{R_L}$$

$$I_L = \frac{4.6V_{pp}}{6.8k} \approx 676.47mA$$

$$2) \text{ set } I_C = 2.5 * I_L$$

$$I_C = (2.5)(676.47)mA$$

$$I_C \approx 1.69mA$$

$$3) \frac{V_{CC}}{2} = V_{CC} - R_C I_C$$

$$5 = 10 - R_C(1.69mA)$$

CE5 specs:

$$R_L \quad 6.8k \quad \pm 5\%$$

$$A_v \quad 40 \frac{V}{V} \quad \pm 10\%$$

$$V_{CC} \quad 10V \quad \pm 5\%$$

$$V_{out,max} \quad 4.6V_{p-p} \quad \geq$$

$$R_{in} \quad 3.6k \quad \geq$$

$$5 = R_C(1.69mA)$$

$$R_C \approx 2.957k\Omega$$

$$4) 1V \approx I_C (R_{EA} + R_{EB})$$

$$591.3 \approx R_{EA} + R_{EB} \approx R_E$$

$$5) 40 \frac{V}{V} = \frac{2.957k}{R_{EA}}$$

$$R_{EA} = \frac{2.957k}{40} = 73.913\Omega$$

$$6) R_{EB} = 591.3 - 73.913 = 517.39\Omega$$

$$7) V_B = V_E + V_{BE} = 1V + .7 = 1.7V$$

$$8) I_B = \frac{I_C}{\beta} \quad \text{worst case } \beta \approx 225$$

$$I_B = \frac{1.69mA}{225} \approx 7.511\mu A$$

$$9) V_B = \frac{R_2}{R_1 + R_2} \cdot V_{CC}$$

$$(.17)^{-1} = \frac{R_1}{R_2}, \quad 4.8824 = \frac{R_1}{R_2}$$

$$R_1 = R_2 \cdot 4.8824$$

$$\text{check } \frac{V_{CC}}{R_1 + R_2} \gg I_B \text{ by about 10 fold}$$

$$591.94\mu A \gg 7.511\mu A$$

50 fold

$$R_{in} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$3.6k = \left( \frac{1}{4.8824 R_2} + \frac{1}{R_2} \right)^{-1}$$

$$(3.6k)^{-1} = \frac{1}{4.8824 R_2} + \frac{1}{R_2}$$

$$R_2 (3.6k)^{-1} = \frac{1}{4.8824} + 1$$


$$R_2 (3.6k)^{-1} = 1.2046173$$

$$R_2 = 4.3373k\Omega$$

$$R_1 = 21.17664k\Omega$$


## SPICE SIMULATION

STEP 2.

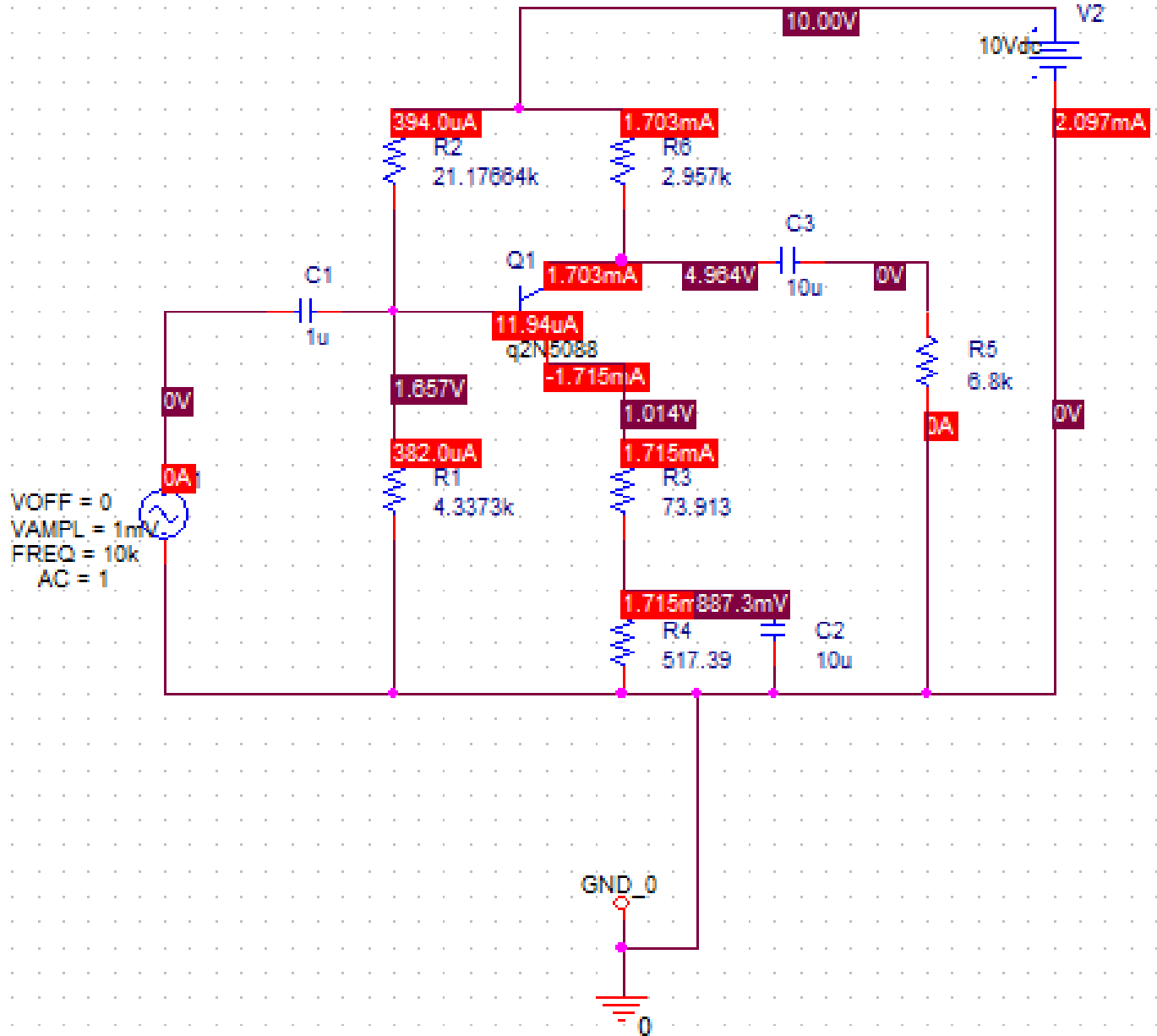


Copy and paste the GND\_0 circle in order to connect the Analog GND to the appropriate wires in your circuit.

STEP 3.

 


In the mid band we're seeing 2.19 Volts out when there is 50 millivolts coming in.  $\frac{2.19V}{50mV} \cong 43.8 \frac{V}{V}$   
 -3Db point @ roughly 250Hz

STEP 4.

 


This is again at 50mV p-p in.

## STEP 5.

 


I could not understand what the appendix was asking of us so Instead I used two traces and the division function to check for maximum input resistance.  $V_b / I_b$ . This seemed like a good idea but the value was roughly 2.6k instead of the parallel combination of resistors connected to the base, which was 3.6k so the idea is flawed.

## STEP 6.

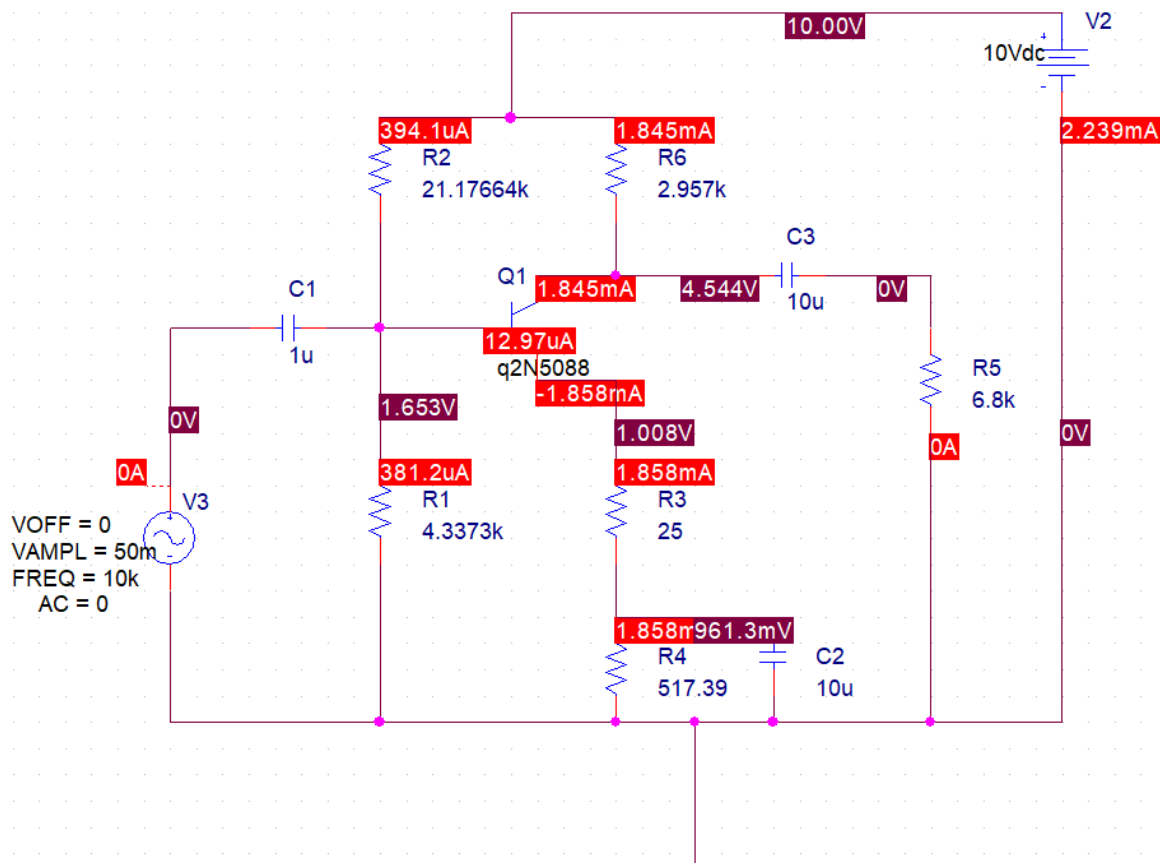


Changing R3 to about a third of the original value allowed us to exceed specs (in simulation). Note that Vc is now roughly 4.5V instead of 5V.


## STEP 7.

 

 (Cursor is further left than it should be. Initially forgot half power point is -3db is .707 times the max)  
CE -3db point at 350Hz



 Cursor is further left than it should be. Initially forgot half power point is -3db is .707 times the max)  
CIN -3db point at 50Hz



Cursor is further left than it should be. Initially forgot half power point is -3db is .707 times the max)  
COUT -3db point at 1.3Hz



## EXPERIMENT

### STEP 8.



Step 8)  $I_c = \frac{V_{ac}}{R_c} = \frac{4.997V}{2.98k} = 3.355mA$

$$V_c = 5.1895$$


$$V_B = 1.5V$$

$$V_E = 870.66mV$$

This is reasonably close given the deviation from the original design.

 
### STEP 9.

Using a frequency of 10k (found during SPICE simulation), the snapshot in step 8 has the following characteristics:




$$\frac{2.04V}{53.5mV} \cong 38.13 \frac{V}{V}$$

## STEP 10.

 

Was a slight bit unsure what the instructions meant to look for here as well. At first I thought clipping was the goal but after playing around with the input amplitude some slew rate becomes visible and that seems more like what was asked. Here, it started to become apparent around 90mV.

## STEP 11.

 


(In our design, both 10 micro Farad capacitors were polarized) The lower -3db frequency we found was at 700Hz, about twice that of CE.

## CONCLUSIONS
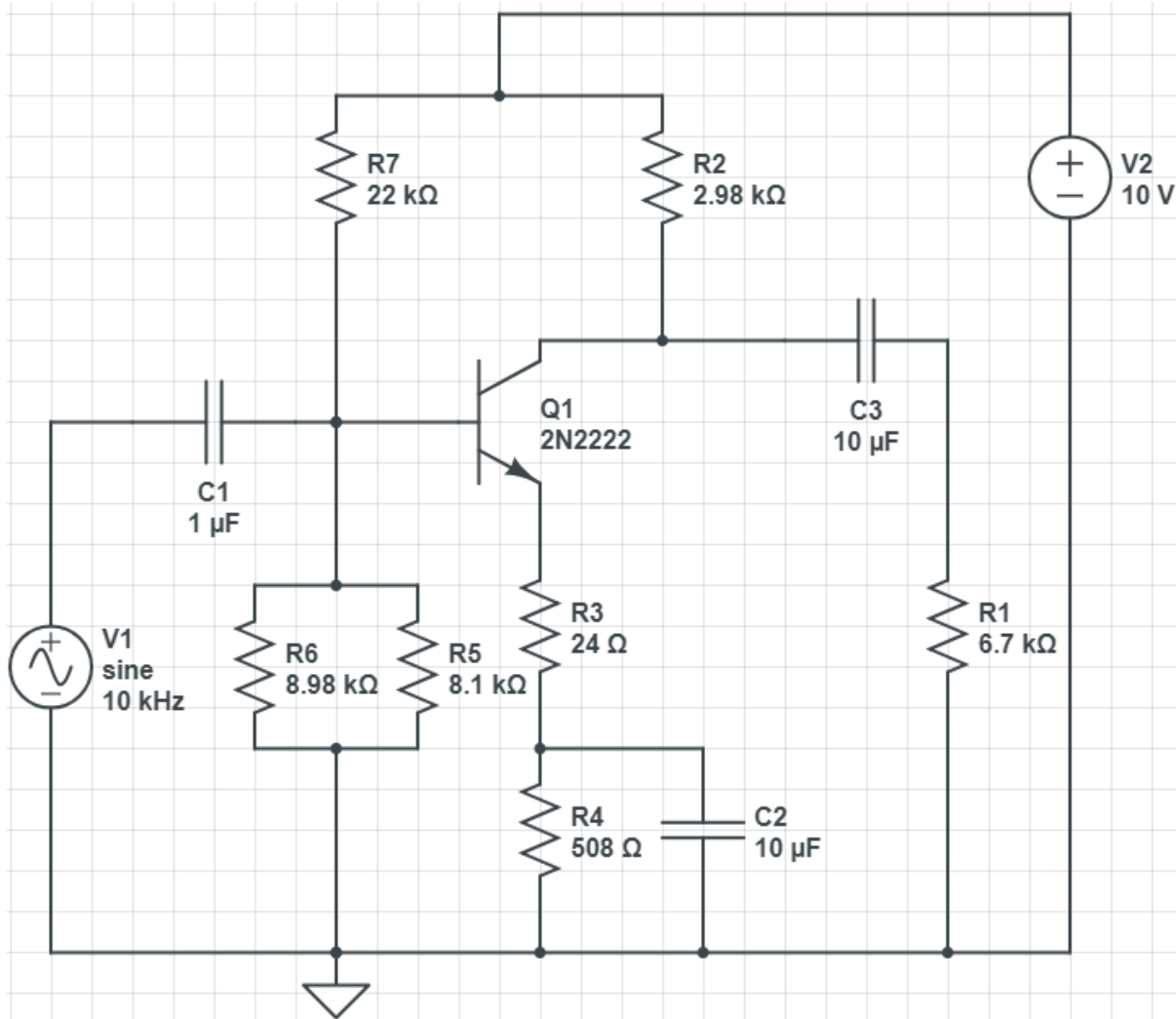
### Item 1.

**Item 1.** Present your final design in the form of a schematic diagram with all part values labeled. State the specifications for gain and output voltage swing, along with the given specifications. State the collector current and the value of  $V_{BB}$ .



Gain: 38.13 V/V  
 Out swing: 4.6V  
 $I_c$ : 3.355mA  
 $V_{BB}$  (V1): 50mV

Set CE5	Load Resistance	$R_L$	6.8k	Ω	±5%
	Voltage gain	$v_o/v_s$	40	V/V	±10%
	Power supply voltage	$V_{CC}$	10	V	±5%
	Minimum swing capability	$v_{out\ max}$	4.6	V <sub>pp</sub>	≥ spec.
	Input Resistance	$R_{in}$	3.6k	Ω	≥ spec.

## APPENDIX A

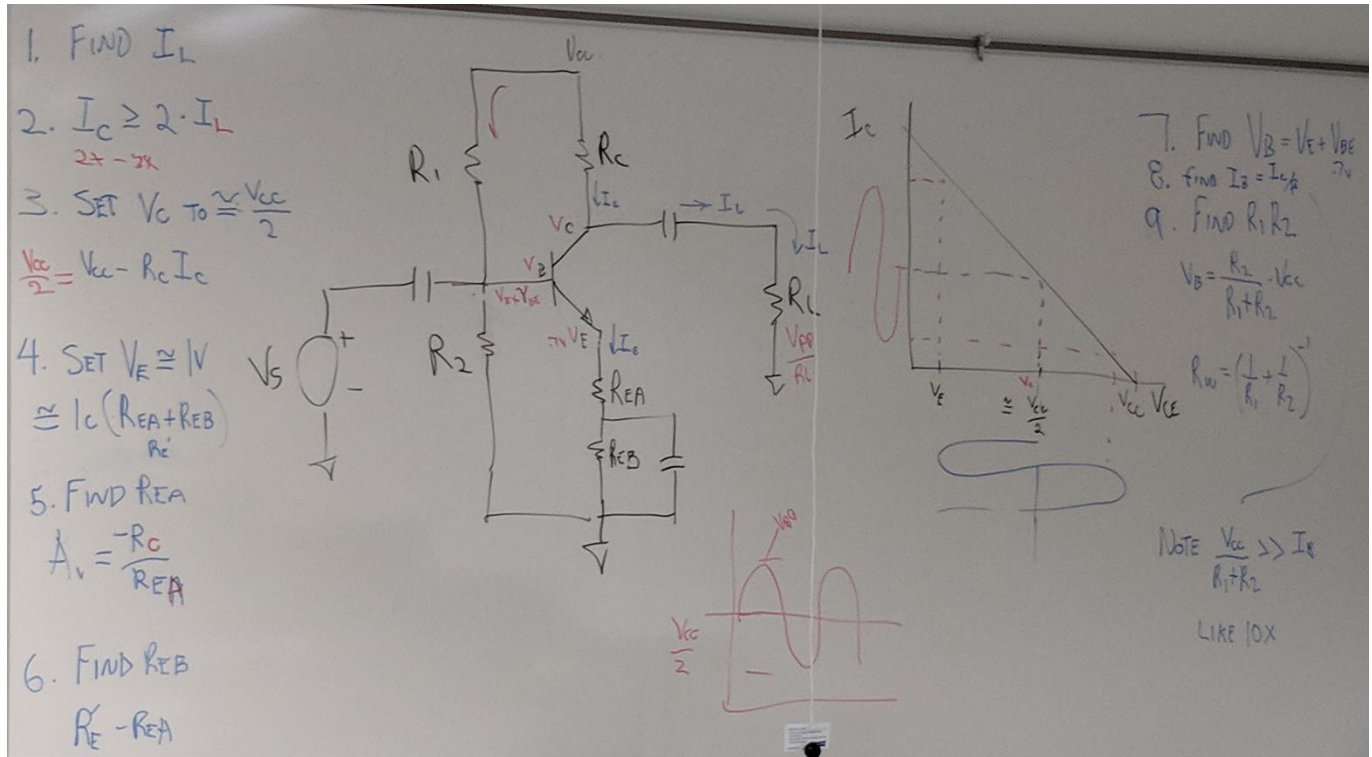


FIGURE 1